

## Experiment Number -02

PEC-101/201 Fundamental of Electronics Engineering Lab  
Er. Yadendra Sharan  
Assistant Professor  
Department of Electrical & Electronics Engineering  
Phonics Group of Institutions, Roorkee  
Phone: +91-8273990016  
[yadvendra.sharan@yahoo.com](mailto:yadvendra.sharan@yahoo.com)

### OBJECT

To study the Logic Gates (AND, OR, NOT and EX-OR)

### APPARATUS REQUIRED

1. Logic Gates Kit.
2. Connecting Probes (Leads).
3. Power Supply

### THEORY

#### 1. AND GATE

The output state of a “Logic AND Gate” only returns “LOW” again when ANY of its inputs are at a logic level “0”. In other words for a logic AND gate, any LOW input will give a LOW output. The logic or Boolean expression given for a digital logic AND gate is that for *Logical Multiplication* which is denoted by a single dot or full stop symbol, ( . ) giving us the Boolean expression of:  $A \cdot B = Y$ .


Then we can define the operation of a 2-input logic AND gate as being:

“If both A and B are true, then Y is true”

#### 2. OR GATE

The output, Q of a “Logic OR Gate” only returns “LOW” again when ALL of its inputs are at a logic level “0”. In other words for a logic OR gate, any “HIGH” input will give a “HIGH”, logic level “1” output.

2-input AND gate

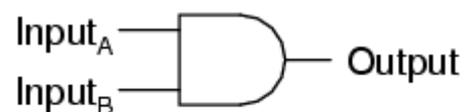

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

The logic or Boolean expression given for a digital logic OR gate is that for *Logical Addition* which is denoted by a plus sign, (+) giving us the Boolean expression of:  $A+B = Y$ .

Then we can define the operation of a 2-input logic OR gate as being:

**“If either A or B is true, then Y is true”**

### 3. NOT GATE

It is a single input device which has an output level that is normally at logic level “1” and goes “LOW” to a logic level “0” when its single input is at logic level “1”, in other words it “inverts” (complements) its input signal. The output from a NOT gate only returns “HIGH” again when its input is at logic level “0”

giving us the Boolean expression of:  $\bar{A} = Y$ .

Then we can define the operation of a single input digital logic NOT gate as being:

**“If A is NOT true, then Y is true”**


### 4. EX-OR GATE

This ability of the *Exclusive-OR gate* to compare two logic levels and produce an output value dependent upon the input condition is very useful in computational logic circuits as it gives us the following Boolean expression of:

$$Y = (A \oplus B) = A.B + A.\bar{B}$$


The logic function implemented by a 2-input Ex-OR is given as either: “A OR B but NOT both” will give an output at Q. In general, an Ex-OR gate will give an output value of logic “1” ONLY when there are an **ODD** number of 1’s on the inputs to the gate, if the two numbers are equal, the output is “0”.

2-input OR gate

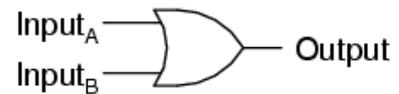

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

NOT gate truth table

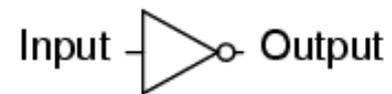

Input	Output
0	1
1	0

Exclusive-OR gate



A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Then an Ex-OR function with more than two inputs is called an “odd function” or modulo-2-sum (Mod-2-SUM), not an Ex-OR. This description can be expanded to apply to any number of individual inputs as shown below for a 3-input Ex-OR gate.

### **PROCEDURE**

Make connections on the Logic Gates Kit and verify the truth table for each logic gate.

### **RESULT**

Successfully studied the Logic Gates and verified the truth table for each Logic Gates.

### **DISCUSSION**

Concept of the digital logic gates is cleared after performing this experiment.

### **PRECAUTIONS**

1. Connections should be proper and tight.
2. Switch “ON” the power after completing the circuit.
3. Carefully read the Logic “High” and Logic “Low” condition.