

## Assignment Number -03

TEC-101/201 Fundamental of Electronics Engineering

Er. Yadvendra Sharan

Assistant Professor

Department of Electrical & Electronics Engineering

Phonics Group of Institutions, Roorkee

Phone: +91-8273990016

[yadvendra.sharan@yahoo.com](mailto:yadvendra.sharan@yahoo.com)

[yadvendrasharan.wordpress.com](http://yadvendrasharan.wordpress.com)

1. What is rectifier? Explain the working of half wave rectifier with neat diagram.
2. Explain clippers circuits? Explain the working of any one with a suitable diagram.
3. Explain clamper circuits? Explain the working of any one with a suitable diagram.
4. What is voltage regulator? Explain its working in detail.